



Fig. 9-8—Circuit diagram of the crystal-filter sideband generator. Unless specified otherwise, capacitances are in  $\mu\mu\text{f.}$ , decimal capacitances are in  $\mu\text{f.}$ , resistors are  $\frac{1}{2}$  watt, resistances are in ohms. Capacitors marked with polarity are electrolytic.

- C<sub>1</sub>—15- $\mu\mu\text{f.}$  differential capacitor (Johnson 160-308).
- C<sub>2</sub>—Dual 50- $\mu\mu\text{f.}$  variable (Johnson 167-52).
- C<sub>3</sub>—Dual 50- $\mu\mu\text{f.}$  variable (Hammarlund HFD-50). Each section has 30- $\mu\mu\text{f.}$  mica compression trimmer in parallel.
- C<sub>4</sub>—50- $\mu\mu\text{f.}$  miniature variable (Hammarlund APC-50B).
- C<sub>5</sub>—11- $\mu\mu\text{f.}$  variable (Johnson 167-1).
- C<sub>6</sub>—100- $\mu\mu\text{f.}$  variable (Hammarlund HFA-100A).
- C<sub>7</sub>—Mounted in L<sub>8</sub> form. See coil table.
- C<sub>8</sub>—365- $\mu\mu\text{f.}$  midget variable (Allied Radio 61 H 009 or Lafayette Radio MS-214).
- CR<sub>1</sub>-CR<sub>13</sub>—400 p.i.v. 500-ma. silicon (Lafayette Radio SP-196).
- FL<sub>1</sub>—9.0-Mc. crystal filter (McCoy Electronics 32 B1).
- J<sub>1</sub>—Microphone jack (Amphenol 75 PC-1M).
- J<sub>2</sub>—Coaxial receptacle (SO-239).
- J<sub>3</sub>—Phono jack.
- J<sub>4</sub>—Open-circuit phone jack.

- L<sub>1</sub>, L<sub>2</sub>—3.1-6.8- $\mu\text{h.}$  variable inductor (Miller M-4405). Coupling coils are 4 t. No. 22 enam. close-wound over center of L<sub>1</sub> and "cold" end of L<sub>2</sub>.
- L<sub>3</sub>-L<sub>7</sub>—See coil table, next page.
- L<sub>8</sub>—5-henry 100-ma. choke (Stancor C-2305).
- L<sub>9</sub>—2-henry 200-ma. choke (Stancor C-2325).
- P<sub>1</sub>—Line plug, preferably fused, 1½ amp.
- RFC<sub>1</sub>—5 t. No. 22 spacewound on 100-ohm 1-watt resistor.
- S<sub>1</sub>—2-pole 6-pos. (2 used) rotary (Centralab PA-2003).
- S<sub>2</sub>—S.p.s.t. toggle.
- S<sub>3</sub>—4-pole 5-position (4 used) 2-section rotary switch (Centralab PA-1013).
- T<sub>1</sub>—800 v.c.t. 200-ma. power transformer with 6.3- and 5-v. filament windings (Knight 61 G 414).
- T<sub>2</sub>—6.3-v.0.6-amp. fil. transformer (Knight 61 G 416).
- Y<sub>1</sub>—See coil table, next page.

provides 700 volts for the output stage, 300 volts for the low-level stages, and regulated 150 volts for the oscillators. Inexpensive silicon rectifiers are used in a combination circuit that provides a basic 700 and 300 volts under load. A small filament transformer, T<sub>2</sub>, is connected to the (otherwise) unused 5-volt winding of the power transformer, and the resulting 90 volts at the secondary is rectified to furnish the bias voltage for the output stage.

The mode switch, S<sub>3</sub>, turns on the power supply, and places the transmitter in readiness to be controlled at J<sub>4</sub>. In its third position, S<sub>3</sub> unbal-

ances the balanced modulator but keeps the output stage biased off, for calibration purposes, and in the fourth position it unbalances the modulator and turns on the final, for tune-up purposes.

**Construction**

The transmitter is built on a 10 × 14 × 3-inch aluminum chassis, with front and rear panels made of sturdy sheet aluminum 9 inches high. The cane-metal sides are bolted to aluminum angle stock that is bolted to the panels; this can be seen in Figs. 9-7 and 9-9. A lip bent inward